

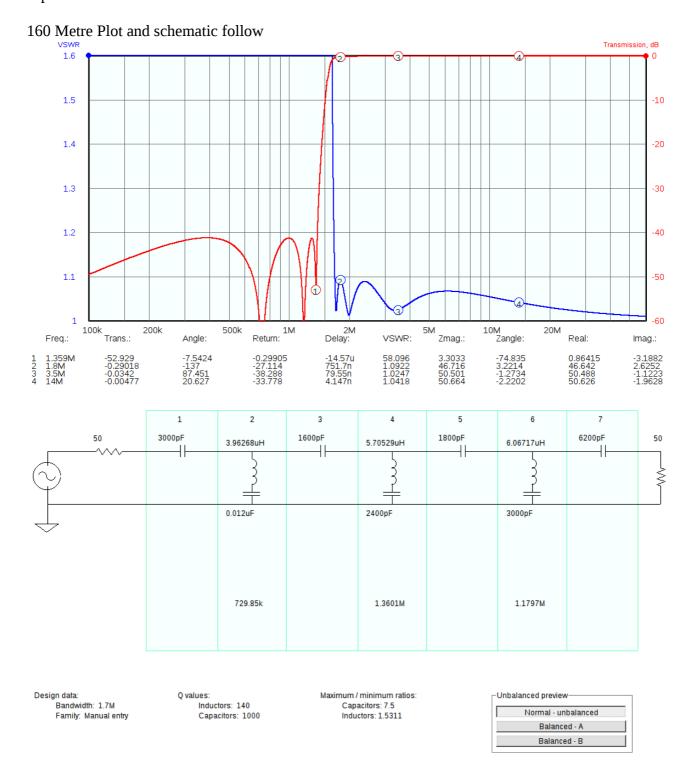
The following are a set of plots for suitable Hi pass filters for Hermes lite. All filters are 5 pole Cauer and designed with a maximum of 2 E12 caps in parallel but in most cases will be a single capacitor.



80 Metre Plot and schematic follow

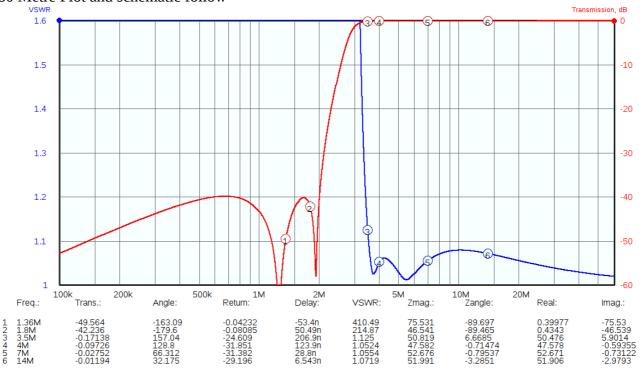

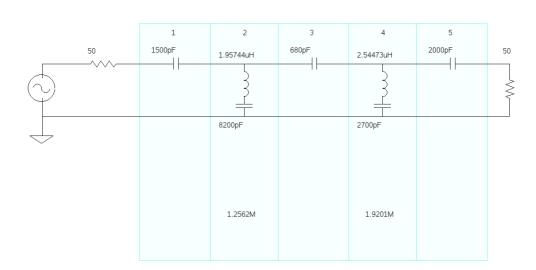

Design data: Bandwidth: 3.4M Family: Manual entry

Inductors: 140
Capacitors: 1000


Maximum / minimum ratios: Capacitors: 12.059 Inductors: 1.3 -Unbalanced preview


Normal - unbalanced

Balanced - A

Balanced - B

40 Metre Plot and schematic follow

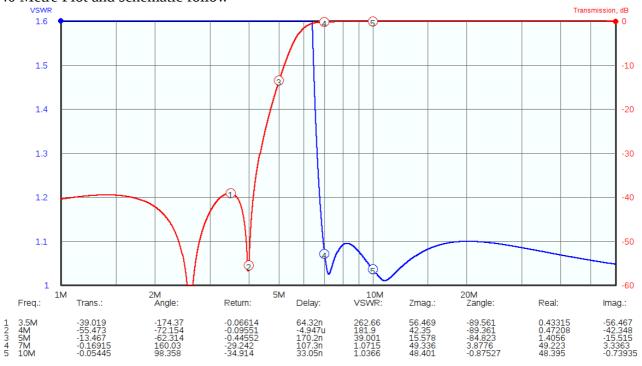

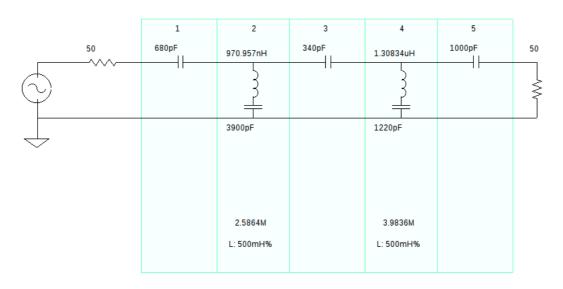


Design data: Bandwidth: 6.9M Family: Manual entry Q values: Inductors: 140 Capacitors: 1000 Maximum / minimum ratios: Capacitors: 11.471 Inductors: 1.3475 Unbalanced preview


Normal - unbalanced

Balanced - A

Balanced - B

30-20 Metre Plot and schematic follow

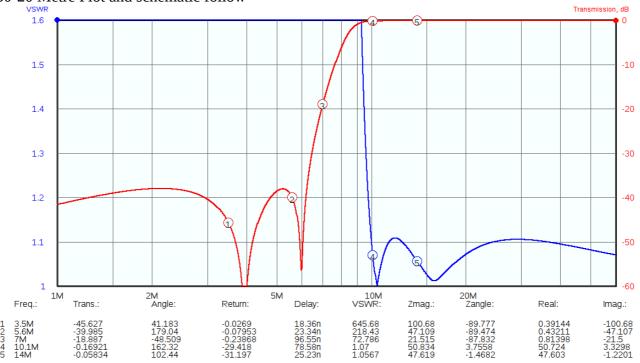

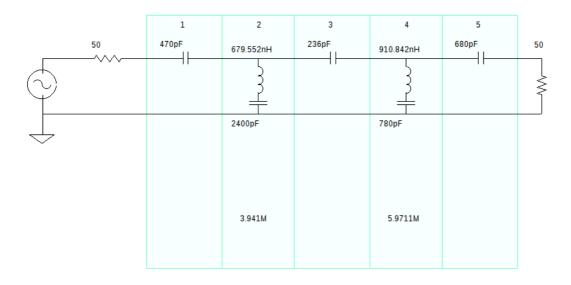



Design data: Bandwidth: 10M Family: Manual entry

Inductors: 150 Capacitors: 1000 Maximum / minimum ratios: Capacitors: 10.169 Inductors: 1.3404

	•	ы		VIE	CV	V					
n	m	na	al-	- U	ın	ba	lan	ce	d		
E	В	3a	ala	an	ce	ed ·	- A				
E	В	3a	ıla	anı	ce	ed -	- B				
	=			_							

17-15 Metre Plot and schematic follow

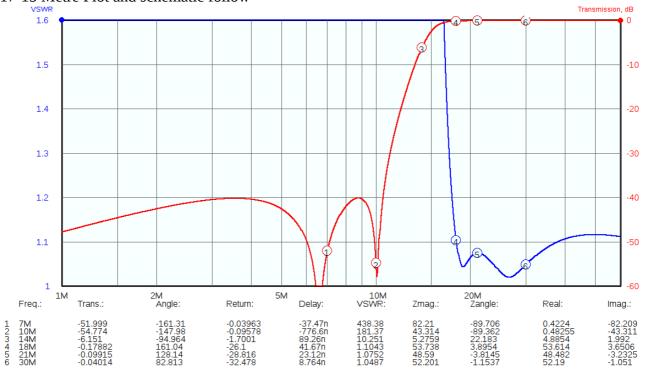

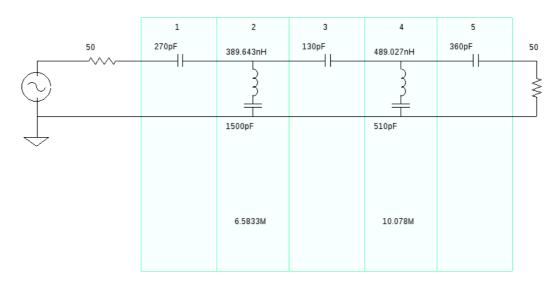


Design data: Bandwidth: 18.06M Family: Manual entry Q values: Inductors: 140 Capacitors: 1000 Maximum / minimum ratios: Capacitors: 11.538 Inductors: 1.2551 Unbalanced preview


Normal - unbalanced

Balanced - A

Balanced - B

12-10 Metre Plot and schematic follow

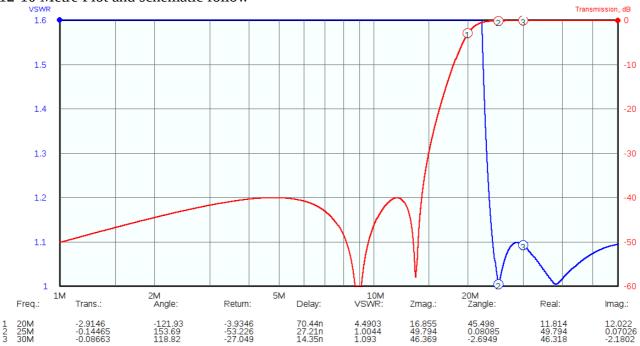

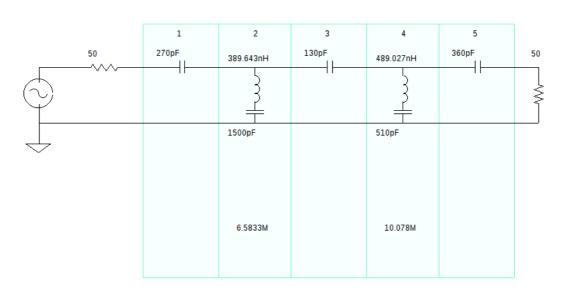

Design data: Bandwidth: 18.06M Family: Manual entry Q values: Inductors: 140 Capacitors: 1000 Maximum / minimum ratios: Capacitors: 11.538 Inductors: 1.2551

-Unbalanced preview
Normal - unbalanced
Balanced - A
Balanced - B