

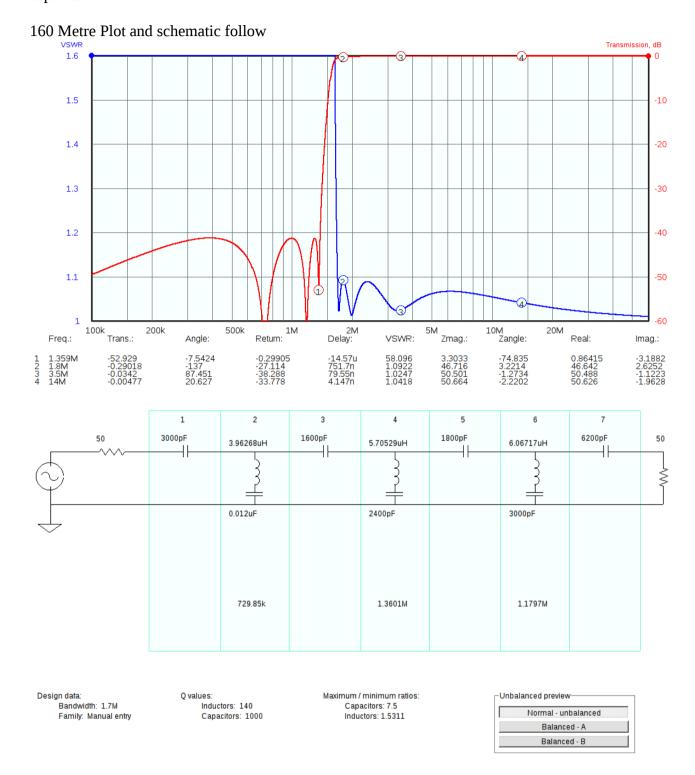
The following are a set of plots for suitable Hi pass filters for Hermes lite. All filters are 5 pole Cauer and designed with a maximum of 2 E12 caps in parallel but in most cases will be a single capacitor.




80 Metre Plot and schematic follow

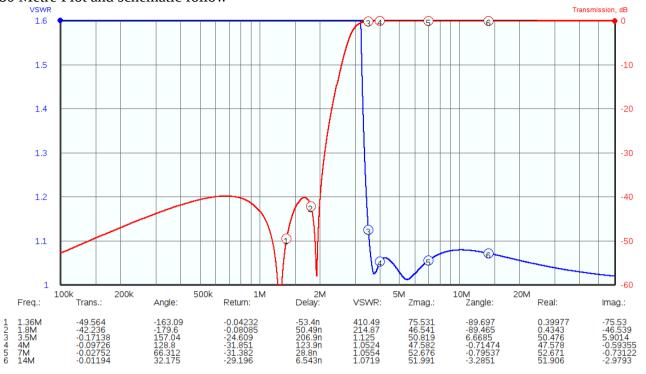


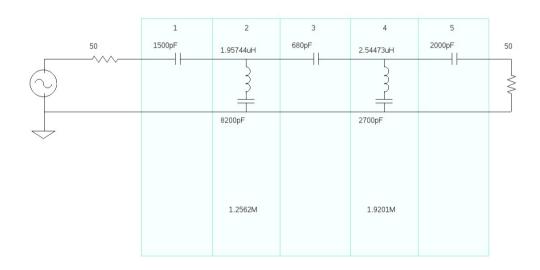

Design data: Bandwidth: 3.4M Family: Manual entry Q values: Inductors: 140 Capacitors: 1000 Maximum / minimum ratios: Capacitors: 12.059 Inductors: 1.3 -Unbalanced preview
Normal - unbalanced
Balanced - A
Balanced - B


40 Metre Plot and schematic follow

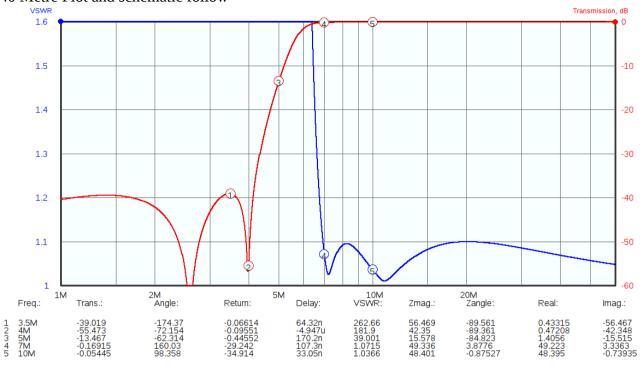


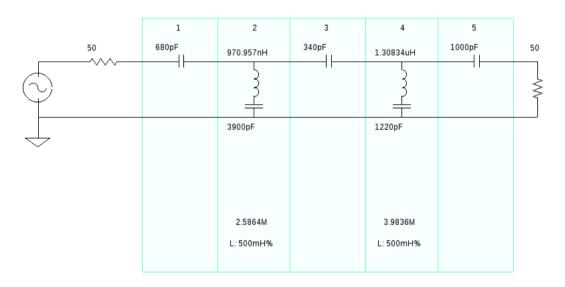

Design data: Bandwidth: 6.9M Family: Manual entry Q values: Inductors: 140 Capacitors: 1000 Maximum / minimum ratios: Capacitors: 11.471 Inductors: 1.3475 - Unbalanced preview
Normal - unbalanced
Balanced - A
Balanced - B


30-20 Metre Plot and schematic follow

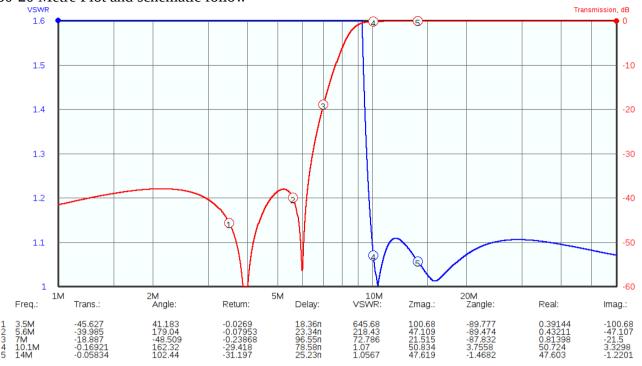


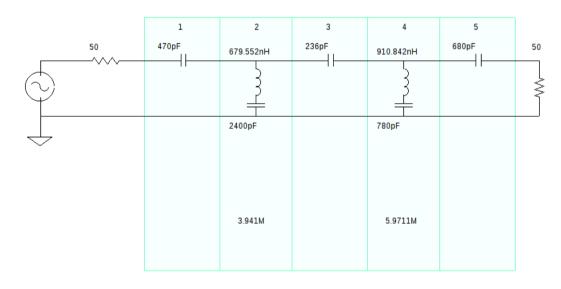

Design data: Bandwidth: 10M Family: Manual entry Q values: Inductors: 150 Capacitors: 1000 Maximum / minimum ratios: Capacitors: 10.169 Inductors: 1.3404 -Unbalanced preview-Normal - unbalanced Balanced - A Balanced - B

17-15 Metre Plot and schematic follow

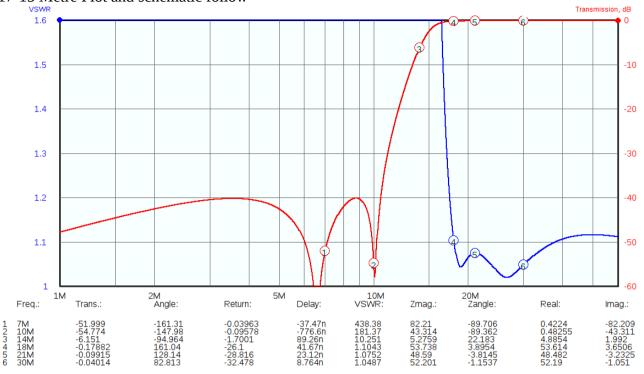

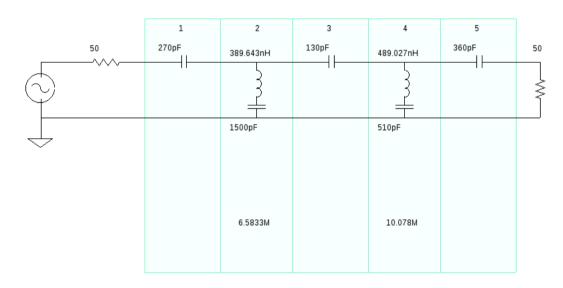


Design data: Bandwidth: 18.06M Family: Manual entry Q values: Inductors: 140 Capacitors: 1000 Maximum / minimum ratios: Capacitors: 11.538 Inductors: 1.2551


Normal - unbalanced

Balanced - A

Balanced - B

12-10 Metre Plot and schematic follow

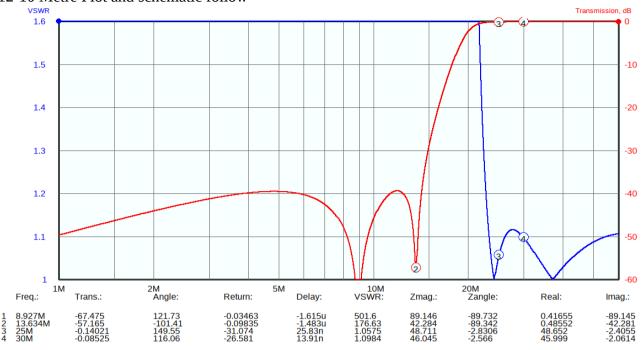

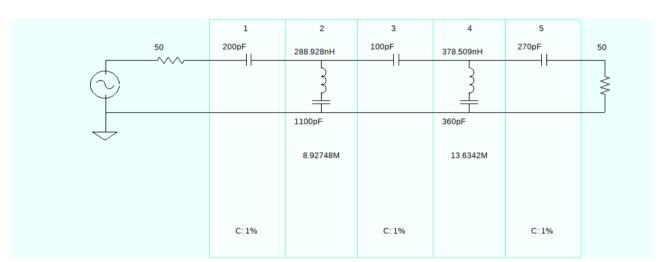

Design data: Bandwidth: 24M Family: Manual entry Q values: Inductors: 140 Capacitors: 1000

Show Q-value resistances?

No
 Yes

Maximum / minimum ratios: Capacitors: 11 Inductors: 1.31

Largest capacitor: 1100pF Smallest capacitor: 100pF

Largest inductor: 378.509nH Smallest inductor: 288.928nH Unbalanced preview

Normal - unbalanced

Balanced